



Cypress Semiconductor

CY7B991-7JXCT

Gawo la Nambala:

Wopanga / Chinthu:

Mafotokozedwe Akatundu

Datasheets:

Mkhalidwe wa RoHS

Zolembe

Chombo Chochokera

Njira Yopereker

CY7B991-7JXCT

Cypress Semiconductor

IC CLK BUFFER 8:8 80MHZ 32PLCC

[CY7B991-7JXCT.pdf](#)

Kutsogolera / RoHS Kumvera

4675 pcs stock

Hong Kong

DHL/Fedex/TNT/UPS/EMS

PEMPHO LA QUOTATION

Chithunzi chingakhale choyimira. Onani ndondomeko zogwiritsira ntchito mankhwala.

Mafotokozedwe a CY7B991-7JXCT

GAWO LA NAMBALA	CY7B991-7JXCT
WOPANGA	Cypress Semiconductor
KUFOTOKOZERA	IC CLK BUFFER 8:8 80MHZ 32PLCC
MKHALIDWE WOPANDA UFULU / MKHALIDWE WA ROHS	Kutsogolera / RoHS Kumvera
CHIWERENGERO CHIPEZEKA	4675 pcs
TSAMBA LAZAMBIRI	CY7B991-7JXCT.pdf
MPHAMVU - ZOPEREKA	4.5 V ~ 5.5 V
LEMBANI	Buffer/Driver
PHUKUSI LA CHIPANGIZO CHOTHANDIZIRA	32-PLCC (11.43x13.97)
MNDANDANDA	RoboClock™
KUGWIRIZANA - KULOWETSA: KUChOKERA	8:8
KUPAKA	Tape & Reel (TR)
PHUKUSI / MLANDUWU	32-LCC (J-Lead)
ZOTSATIRA	TTL
KUTENTHA KWAMBIRI	0°C ~ 70°C
CHIWERENGERO CHA MAULENDO	1
MTUNDU WOKWERA	Surface Mount
MPHUNO YOPANDA CHISOKONEZO (MSL)	3 (168 Hours)
MKHALIDWE WOPANDA UFULU / MKHALIDWE WA ROHS	Lead free / RoHS Compliant
KULOWETSA	3-State, TTL
MAULENDO - MAX	80MHz
KUSIYANITSA - KULOWETSA: KUTULUKA	Yes/Yes
KUFOTOKOZEDWA KWAMBIRI	Clock Buffer/Driver IC 8:8 80MHz 32-LCC (J-Lead)
CHIGAWO CHOYAMBIRA	CY7B991

Matanthauzo okhudzana

Cypress Semiconductor CY7B991-7JXCT	AAAA Distributor	CY7B991-7JXCT Wopereka
CY7B991-7JXCT Mtengo	CY7B991-7JXCT Zithunzi	CY7B991-7JXCT Image
CY7B991-7JXCT PDF Datasheet	CY7B991-7JXCT Dinani Datasheet	CY7B991-7JXCT Datasheet
CY7B991-7JXCT Stock	Gulani CY7B991-7JXCT	Gulani Cypress Semiconductor CY7B991-7JXCT
Cypress Semiconductor CY7B991-7JXCT	Cypress Semiconductor Wogulitsa	Cypress Semiconductor Distributor
Cypress Semiconductor CY7B991-7JXCT	Cypress Semiconductor Corp CY7B991-7JXCT	

Zogwirizana

<p>CY7B991-5JXI Opanga: Cypress Semiconductor Kufotokozera: IC CLK BUFFER 8:8 80MHZ 32PLCC Zilipo: 3561 pcs RFQ</p>	<p>CY7B991-7JI Opanga: Cypress Semiconductor Kufotokozera: IC CLK BUFFER 8:8 80MHZ 32PLCC Zilipo: 5597 pcs RFQ</p>
<p>CY7B9910-2SXC Opanga: Cypress Semiconductor Kufotokozera: IC CLK BUFF SKEW 8OUT 24SOIC Zilipo: 4983 pcs RFQ</p>	<p>CY7B991-5JXCT Opanga: Cypress Semiconductor Kufotokozera: IC CLK BUFFER 8:8 80MHZ 32PLCC Zilipo: 6118 pcs RFQ</p>
<p>CY7B991-5JXIT Opanga: Cypress Semiconductor Kufotokozera: IC CLK BUFFER 8:8 80MHZ 32PLCC Zilipo: 4035 pcs RFQ</p>	<p>CY7B991-7JC Opanga: Cypress Semiconductor Kufotokozera: IC CLK BUFFER 8:8 80MHZ 32PLCC Zilipo: 7037 pcs RFQ</p>
<p>CY7B9910-5SI Opanga: Cypress Semiconductor Kufotokozera: IC CLK BUFF SKEW 8OUT 24SOIC Zilipo: 7881 pcs RFQ</p>	<p>CY7B9910-2SXC Opanga: Cypress Semiconductor Kufotokozera: IC CLK BUFF SKEW 8OUT 24SOIC Zilipo: 3367 pcs RFQ</p>
<p>CY7B9910-5SC Opanga: Cypress Semiconductor Kufotokozera: IC CLK BUFF SKEW 8OUT 24SOIC Zilipo: 5611 pcs RFQ</p>	<p>CY7B991-7JXC Opanga: Cypress Semiconductor Kufotokozera: IC CLK BUFFER 8:8 80MHZ 32PLCC Zilipo: 3828 pcs RFQ</p>
<p>CY7B9910-2SC Opanga: Cypress Semiconductor Kufotokozera: IC CLK BUFF SKEW 8OUT 24SOIC Zilipo: 3260 pcs RFQ</p>	<p>CY7B9910-5SXC Opanga: Cypress Semiconductor Kufotokozera: IC CLK BUFF SKEW 8OUT 24SOIC Zilipo: 4944 pcs RFQ</p>